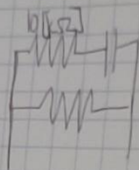


Impedance Spectroscopy

Setup

Cancerous tissue doesn't attach normally and therefore a different impedance.



Input & output frequencies are the same if we have a linear response.

200 Ω D the unlabeled resistor

$\approx 1 \text{ kHz}$

10V \Rightarrow rms = $\frac{1}{\sqrt{2}}$

Sensitivity: 50 mV

Record: f, phase, $V_{out} = V_{rms}$

$\frac{V_{out}}{I} = \text{impedance}$

we need $Z(f)$

Breadboard:

100k $\pm 10\%$

200 Ω (measured)

given: 0.22 μF

measured: 238 nF

20.0 Ω (measured)

20.0 $\Omega \pm 5\%$ (given)

200 $\Omega \pm 5\%$ (given)

197.7 Ω (measured)

f	Phase	V_{out}
1052 Hz	18.9 $^\circ$	13.57 mV
10024 Hz	14.9 $^\circ$	13.73 mV
91098 Hz	15.2 $^\circ$	13.23 mV
10 kHz	2.5 $^\circ$	13.51 mV
79 kHz	0.1 $^\circ$	12.58 mV

Compare with theoretical
Pulse - phase-sensitive measurements

Admittance Spectroscopy we Fitting

71

general form for a circuit shaped like ours
could be:

$$V = I_0 |Z|, |Z| = \sqrt{\text{Re}\{Z\}^2 + \text{Im}\{Z\}^2}$$

$$V = I_0 \sqrt{\text{Re}\{Z\}^2 + \text{Im}\{Z\}^2}$$

$$Z = R_1 \frac{(1 + \omega^2 C^2 R_1(R_1 + R_2)) - j\omega C R_1}{1 + \omega^2 C^2 (R_1 + R_2)^2}$$


$$\text{Re}\{Z\} = R_1 \frac{1 + \omega^2 C^2 R_1(R_1 + R_2)}{1 + \omega^2 C^2 (R_1 + R_2)^2}$$

$$\text{Im}\{Z\} = \frac{-R_1 \omega C}{1 + \omega^2 C^2 (R_1 + R_2)^2}$$

$$V = I_0 \sqrt{\frac{(1 + (2\pi f)^2 C^2 R_1(R_1 + R_2))^2 + ((2\pi f)^2 C R_1)^2}{1 + (2\pi f)^2 C^2 (R_1 + R_2)^2}} R_1$$

$$\phi = \tan^{-1} \frac{-R_1 \omega C}{1 + (2\pi f)^2 C^2 R_1(R_1 + R_2)}$$

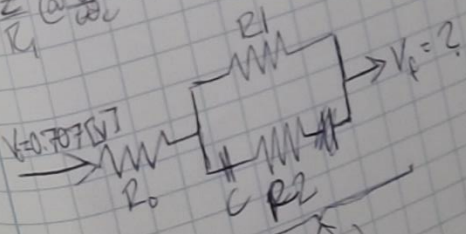if $\frac{Z}{R_1} @ \frac{\omega}{\omega_c} = 1$ then everything will Z ✓



System (under test)

$$\begin{aligned} Z &= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{R_1(R_2 - j\omega C R_2)}{R_1 + R_2 - j\omega C R_2 R_1} \\ &= R_1 \frac{(R_2 - j\omega C R_2)}{R_2 + R_1 - j\omega C R_2 R_1} = R_1 \frac{R_2(1 - j\omega C R_2)}{R_2 + R_1 - j\omega C R_2 R_1} \\ &= R_1 \frac{(1 - j\omega C R_2)(1 + (R_2 + R_1)j\omega C)}{1 + (R_2 + R_1)^2 \omega^2 C^2} \\ &= R_1 \frac{(1 - R_2 R_1 \omega^2 C^2) + j\omega C (R_2 + R_1)(1 - R_2 R_1 \omega^2 C^2)}{1 + (R_2 + R_1)^2 \omega^2 C^2} \\ &= R_1 \frac{1 - R_2 R_1 \omega^2 C^2 + j\omega C (R_2 + R_1)(1 - R_2 R_1 \omega^2 C^2)}{1 + (R_2 + R_1)^2 \omega^2 C^2} \end{aligned}$$

side note: m/m of R_2 b/c it seems to be changing



Data

