



Impedance Spectroscopy

Kitty Harris and Josh Eslarboukh

Frequency Dependence of Impedance

➤ **Impedance** is a measure of how current flow is hindered in a system.

➤ $Z_{series} = \sum_i Z$ and $\frac{1}{Z_{parallel}} = \sum_i \frac{1}{Z}$

➤ $Z_R = R$ and $Z_C = \frac{1}{j\omega C}$


➤ So, for our system under test, we end up with

$$Z = \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right)^{-1} = \left(\frac{1}{R_1} + \frac{1}{\frac{1}{j\omega C} + R_2} \right)^{-1} = \frac{R_1(1 + \omega^2 C^2 R_2(R_1 + R_2)) - j\omega C R_1}{1 + \omega^2 C^2 (R_1 + R_2)^2}$$

➤ As frequency approaches zero, the system behaves more like a DC circuit and charge cannot cross the branch containing the capacitor, so $Z \cong R_1$.


➤ As frequency becomes arbitrarily large, the current can arc across the capacitor, effectively ignoring its presence, and $Z \cong \frac{R_1 R_2}{R_1 + R_2}$.



➤ $V = I|Z|$

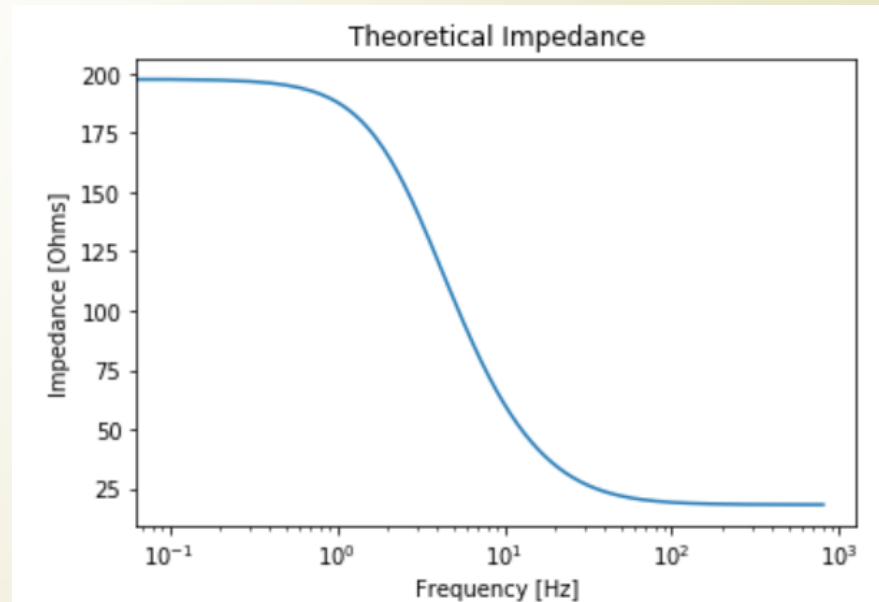

Frequency Meter

- ▶ A digital frequency counter measures frequency by taking counts of a periodic function over a **gate time**.
- ▶ **Direct counting** methods measure how many times the voltage (or other property being measured) passes a given threshold.
- ▶ **Reciprocal** frequency counters measure the period of a cycle and take the inverse.
- ▶ A clock produces a signal which is divided by the **decade dividers** into the appropriate gate time.
- ▶ The “gate flip flop” receives this information and signals when the next set of counts should begin.
- ▶ The **latch** holds the last value so that it can continue to be displayed while the counter is updating based on a new set of data.

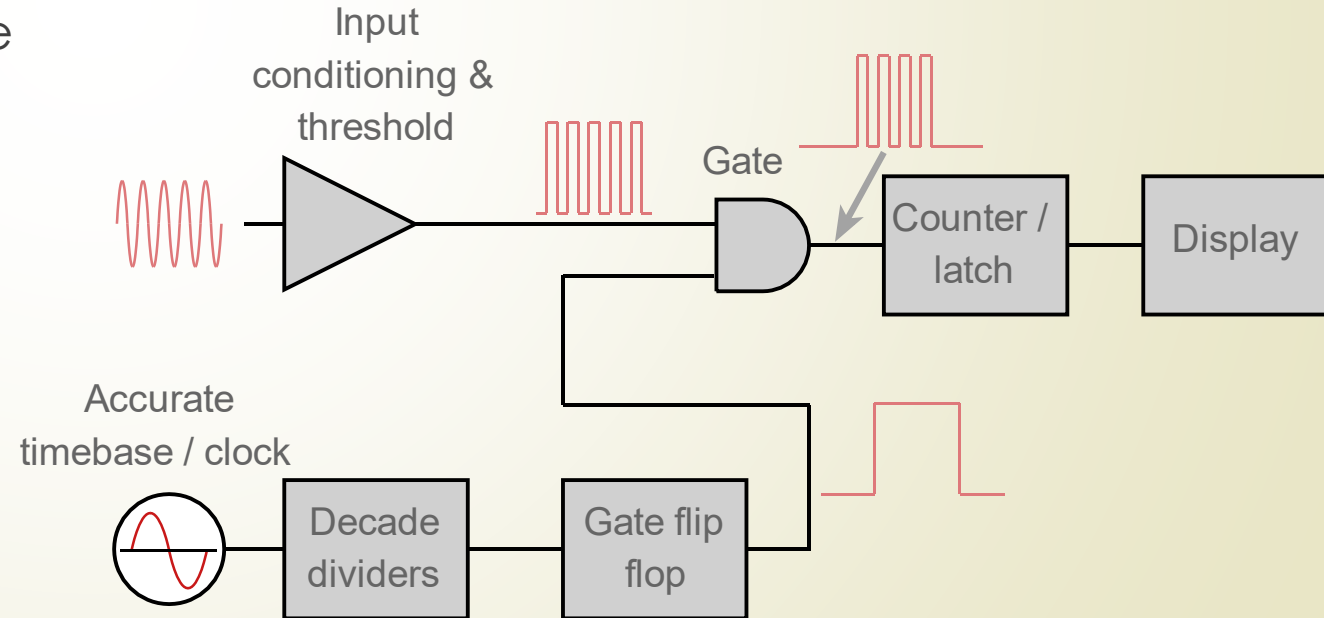

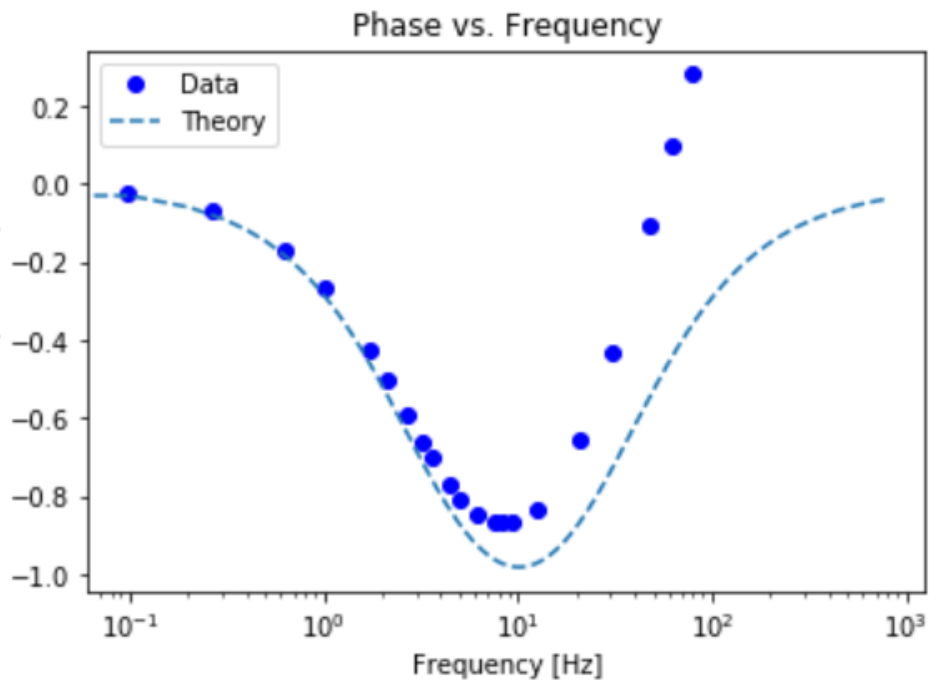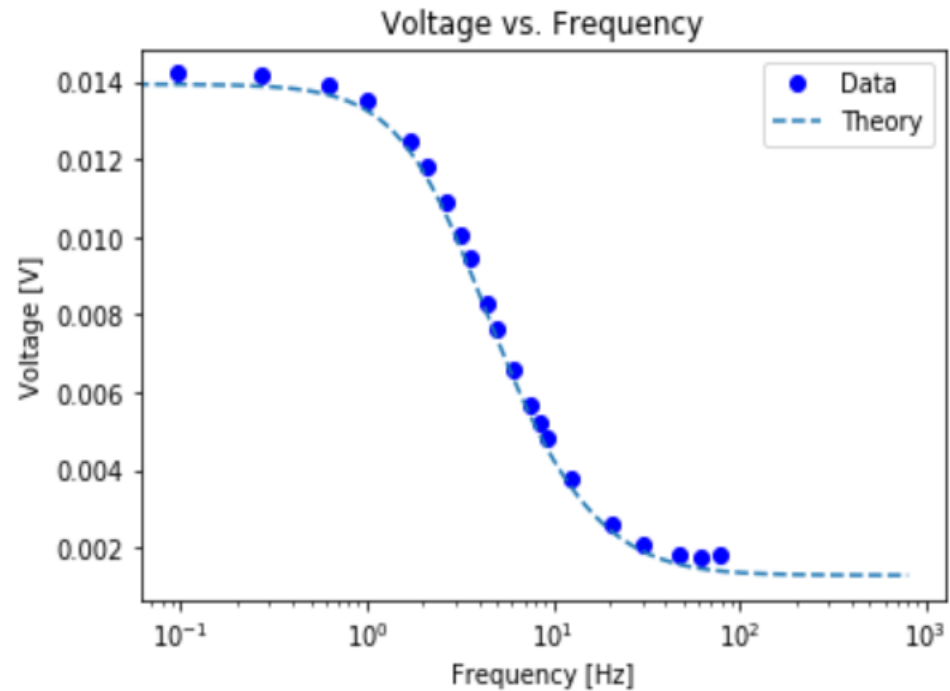

Prediction vs. Data

Voltage Data

- ▶ We see an almost perfect correlation here, especially in the center.
- ▶ Asymptotes match fairly well
- ▶ Standard deviation: $8 \cdot 10^{-8}$ [V]

Phase Data

- ▶ The left half of the plot appears to be roughly correct.
- ▶ The dip occurs at the right point.
- ▶ We have positive phase; this should be impossible with an ideal circuit of our type
- ▶ Possible explanation: Something within the circuit is behaving as an inductor, producing a field opposing the current, causing the positive phase.
- ▶ Standard deviation: 0.05 [radians]



References



How Does a Frequency Counter Work. (n.d.). Retrieved from Electronics Notes:
<https://www.electronics-notes.com/articles/test-methods/frequency-counter-timer/how-does-a-frequency-counter-work-operation.php>

laserjocky. (2014). *Digital Frequency Counter*. Retrieved from instructables:
<https://www.instructables.com/id/Digital-Frequency-Counter/>