

Impedance Spectroscopy

Prelab

2.1) Use $\hat{v} = \hat{V}e^{j\omega t}$ and $\hat{i} = \hat{I}e^{j\omega t}$ to show $Z = \frac{\hat{V}}{\hat{I}} = \frac{1}{j\omega C}$ for a capacitor

$$Z = \frac{\hat{V}}{\hat{I}} = R \quad \hat{v} = C \frac{d\hat{v}}{dt} = C j\omega \hat{V} e^{j\omega t}$$

$$\frac{\hat{V}}{\hat{I}} = \frac{\hat{V} e^{j\omega t}}{\hat{I} e^{j\omega t}} = R \quad \text{so } Z = R = \frac{\hat{V}}{C j\omega \hat{V}} \quad \text{so } Z = \frac{1}{C j\omega}$$

2.2) Verify that $v(t) = \frac{I}{\omega C} \sin(\omega t) = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$ satisfies $i = C \frac{dv}{dt}$ when $i = I \cos(\omega t)$
 $\frac{dv}{dt} = \frac{I}{\omega C} \omega \cos(\omega t)$, so $i = C \frac{dv}{dt} = I \cos(\omega t)$, as desired.

2.3) Show that, for an inductor, $Z = j\omega L$

$$v = L \frac{di}{dt} = L \hat{I} e^{j\omega t} j\omega \quad \frac{v}{i} = Z = L j\omega \quad \text{so } Z = j\omega L$$

2.4) Taking the real part of $\hat{I} Z e^{j\omega t}$ gives $v(t) = -\omega L \sin(\omega t) = \omega L \cos(\omega t + 90^\circ)$.
 Verify this, and that it satisfies $v = L \frac{di}{dt}$ when $i = I \cos(\omega t)$.

$$Z = L j\omega \quad \text{so } \hat{I} Z e^{j\omega t} = L j\omega \hat{I} e^{j\omega t} = L j\omega \hat{I} (\cos(\omega t) + j \sin(\omega t))$$

$$v(t) = L \omega \hat{I} (j \cos(\omega t) - \sin(\omega t)), \quad \text{the real part of which is}$$

$$v_{\text{real}}(t) = -L \omega \hat{I} \sin(\omega t)$$

$$v = L \frac{di}{dt} = L I \omega \sin(\omega t) \quad \checkmark$$

2.5) a) Use trig identities to show that $p_{\text{av}} = \frac{I^2}{2} |Z| [\cos \phi + \cos(2\omega t + \phi)]$

$$\text{We wish to show that } \cos \omega t \cos(\omega t + \phi) = \frac{1}{2} (\cos \phi + \cos(2\omega t + \phi))$$

$$\cos(a+b) = \cos a \cos b - \sin a \sin b$$

$$\cos(\omega t + \phi) = \cos(\omega t) \cos \phi - \sin(\omega t) \sin \phi$$

$$\cos^2(\omega t) \cos \phi - \cos(\omega t) \sin(\omega t) \sin \phi$$

$$\sin a \sin b = \frac{1}{2} (\cos(a-b) - \cos(a+b))$$

$$\sin(\omega t) \sin \phi = \frac{1}{2} (\cos(\omega t - \phi) - \cos(\omega t + \phi))$$

$$\cos^2(\omega t) \cos \phi - \cos(\omega t) \frac{1}{2} (\cos(\omega t - \phi) - \cos(\omega t + \phi))$$

$$\cos a \cos b = \frac{1}{2} (\cos(a-b) + \cos(a+b))$$

Impedance Spectroscopy

Pr e l a b

67

(2.5) (a) $\cos(\omega t) \cos(\omega t - \phi) = \frac{1}{2} (\cos(2\omega t - \phi) + \cos(2\omega t - \phi))$

$$\cos(\omega t) \cos(\omega t + \phi) = \frac{1}{2} (\cos(2\omega t + \phi) + \cos(2\omega t + \phi))$$

$$\cos^2(\omega t) \cos \phi = \frac{1}{4} (\cos(2\omega t - \phi) - \cos(2\omega t + \phi)) = \cos^2(\omega t) \cos \phi + \frac{1}{4} (\cos(2\omega t + \phi) - \cos(2\omega t - \phi))$$

$$\cos a + \cos b = 2 \cos \frac{a+b}{2} \cos \frac{a-b}{2}$$

~~$$\cos a - \cos b = -2 \sin \frac{a+b}{2} \sin \frac{a-b}{2}$$~~

$$\cos^2 a = \frac{1 + \cos(2a)}{2}$$

$$\cos^2(\omega t) = \frac{1 + \cos(2\omega t)}{2}$$

$$\frac{1 + \cos(2\omega t)}{2} \cos \phi + \frac{1}{4} (\cos(2\omega t + \phi) - \cos(2\omega t - \phi))$$

$$\frac{1}{2} \cos \phi + \frac{1}{2} \cos(2\omega t) \cos \phi + \frac{1}{2} \left(\frac{1}{2} (\cos(2\omega t + \phi) - \cos(2\omega t - \phi)) \right)$$

$$\frac{1}{2} \left(\cos \phi + \frac{1}{2} (\cos(2\omega t - \phi) + \cos(2\omega t + \phi)) + \frac{1}{2} (\cos(2\omega t + \phi) - \cos(2\omega t - \phi)) \right)$$

$$= \frac{1}{2} (\cos \phi + \cos(2\omega t + \phi)) \quad \checkmark$$

b) Explain why $P_{eff} \neq R \frac{1}{2} e^{i\omega t} \hat{V} e^{i\omega t} = R i v = v^2 \neq i v$

Because $P_{eff} = i \omega V_{eff} \neq v^2$ unless $v = i$, which it cannot as they have different units

c) Show that $\langle p \rangle = \frac{1}{2} I^2 |Z| \cos \phi$ over one period of oscillation

$$\langle p \rangle = \frac{1}{2} I^2 |Z| (\cos \phi + \langle \cos(2\omega t + \phi) \rangle) = \frac{1}{2} I^2 |Z| \cos \phi$$

This ranges evenly from -1 to 1, making $\langle \rangle \rightarrow 0$.
So, this term simply drops out

d) Show that $\langle p \rangle = \frac{1}{2} R I^2 = \frac{1}{2} I^2 R$

~~$$R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R \neq \frac{1}{2} R$$~~

o $\langle i \omega V_{eff} \rangle = \text{stuff, getting ahead of myself}$

$$P_{eff} = i \omega V_{eff} = I \cos(\omega t) V \cos(\omega t + \phi) = I^2 \cos(\omega t) |Z| \cos(\omega t + \phi) = I^2 |Z| \frac{1}{2} \cos(\phi)$$

$$\langle p \rangle = \frac{1}{2} I^2 |Z| \cos(-\phi) \neq 0, \quad R(Z) = |Z| \cos(-\phi)$$

Impedance Spectroscopy

Prelab

2.6) Show that the average power dissipated in a capacitor filled with a material of relative complex permittivity is given by


$\langle p \rangle = \frac{I^2}{2\omega C} \sin \delta$, where C is the magnitude of the capacitance and δ is the loss angle defined by $\sin \delta \equiv \frac{\epsilon''}{\epsilon'}$ complex-valued.

$$\langle p \rangle = \frac{1}{2} I^2 |Z| \cos(\phi) = \frac{1}{2} I^2 \left| \frac{1}{j\omega \epsilon' \epsilon'' A} \right| = \frac{I^2}{2} \frac{\cos(\phi)}{j\omega C} = \frac{I^2}{2\omega C} \cos(\phi)$$

$$= \frac{I^2}{2\omega C} \sin \delta$$

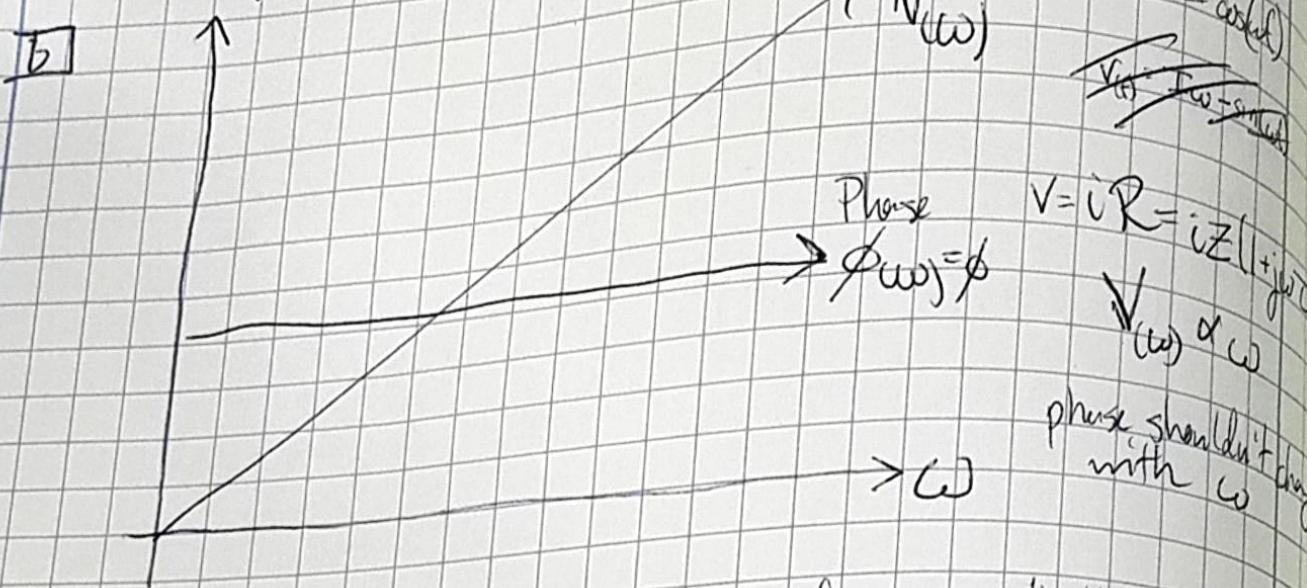2.7) (a) Show that $Z = \frac{R}{1+j\omega\tau}$, where $\tau = RC$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{j\omega C} = \frac{1}{R} + \frac{j\omega R}{j\omega R C} = \frac{j\omega R + 1}{R} = \frac{j\omega\tau + 1}{R} \rightarrow Z = \frac{R}{1+j\omega\tau}$$



2.8) (a) Without analysis, give zero- and high-frequency limits of impedances

~~$Z \rightarrow R$~~ $0: Z \rightarrow R$
 ~~$Z \rightarrow 0$~~ $\infty: Z \rightarrow 0$

(b) Show that the impedance of this circuit can be written as

$$\frac{Z}{R_1} = \frac{1 + j\omega \frac{R_2}{R_1} C}{1 + j\omega C (R_1 + R_2)}, \text{ where } \omega_c = \frac{1}{(R_1 + R_2)C}$$

$$Z = \frac{R_1 + R_2}{1 + j\omega(R_1 + R_2)C} = R_1 \frac{1 + \frac{R_2}{R_1}}{1 + j\omega C (R_1 + R_2)} = \frac{1 + \frac{R_2}{R_1}}{1 + j\omega C (R_1 + R_2)} R_1 \Rightarrow \frac{1 + \frac{R_2}{R_1}}{1 + j\omega C (R_1 + R_2)} = \frac{Z}{R_1}$$

$$\frac{R_2}{R_1} = \frac{R_2}{R_1} \frac{(R_1 + R_2)C}{(R_1 + R_2)C} = \frac{R_2}{\omega_c R_1 C (R_1 + R_2)} = \frac{R_2}{\omega_c R_1} \frac{\omega_c}{R_1 + R_2} = \frac{R_2}{\omega_c R_1} j\omega$$

Impedance Spectroscopy


Pre-lab

(2.8) Find an expression for $\frac{|Z|}{R_1}$. Now suppose $\frac{R_2}{R_1} = 0.1$. Plot $\frac{|Z|}{R_1}$ vs ω/ω_c .

$$|Z| = \frac{R_2 + R_1}{1 + \frac{\omega}{\omega_c}}$$

$$\frac{|Z|}{R_1} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{\omega}{\omega_c}}$$

$$\text{If } \frac{R_2}{R_1} = 0.1 \Rightarrow \frac{|Z|}{R_1} = \frac{1.1}{1 + \frac{\omega}{\omega_c}}$$

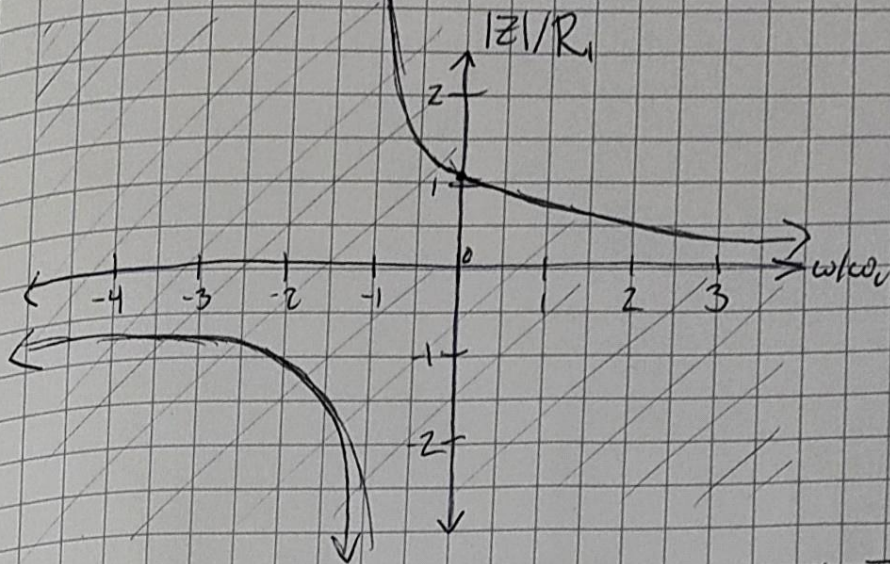

d) Find an expression for the phase ϕ of the impedance ($\tan \phi = \frac{\text{Im} Z}{\text{Re} Z}$)

$$\phi = \tan^{-1} \left(\frac{\text{Im} \left(\frac{1 + \frac{R_2}{R_1}}{1 + \frac{\omega}{\omega_c}} \right)}{\text{Re} \left(\frac{1 + \frac{R_2}{R_1}}{1 + \frac{\omega}{\omega_c}} \right)} \right) = \tan^{-1} \left(\frac{0}{1} \right)$$

