




# Impedance Spectroscopy

Kitty Harris and Josh Eslarboukh
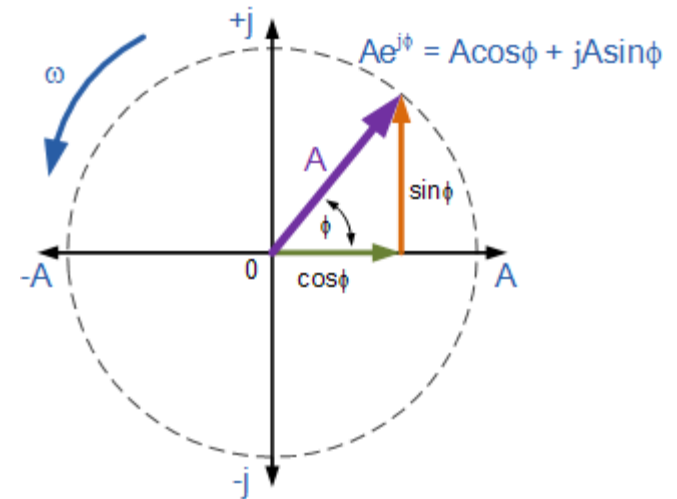
# Phasor Notation

- ▶ Phasors are essentially a shorthand for oscillating functions expressed as functions of their phase and magnitude
- ▶ Name is portmanteau ("phase vector")
- ▶ Consolidates signal information, for example:
  - $e(t) = \sqrt{2} A \cos(\omega t + \phi)$
  - Becomes  $A \angle \phi = A^* e^{j(\omega t + \phi)}$  where  $j = \sqrt{-1}$
- ▶ Allows for use of complex impedance
  - $Z = R + jX$ 
    - $Z$  = total complex impedance
    - $R$  = resistor impedance, "resistance"
    - $X$  = capacitor/inductor impedance, "reactance"
  - Complies with Kirchhoff's circuit laws and Ohm's law of resistivity



# Frequency Dependence of Impedance

➤ **Impedance** is a measure of how current flow is hindered in a system.

➤  $Z_{series} = \sum_i Z$  and  $\frac{1}{Z_{parallel}} = \sum_i \frac{1}{Z}$

➤  $Z_R = R$  and  $Z_C = \frac{1}{j\omega C}$


➤ So, for our system under test, we end up with

$$Z = \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right)^{-1} = \left( \frac{1}{R_1} + \frac{1}{\frac{1}{j\omega C} + R_2} \right)^{-1} = \frac{R_1(1 + \omega^2 C^2 R_2(R_1 + R_2) - j\omega C R_1)}{1 + \omega^2 C^2 (R_1 + R_2)^2}$$

➤ As frequency approaches zero, the system behaves more like a DC circuit and charge cannot cross the branch containing the capacitor, so  $Z \cong R_1$ .


➤ As frequency becomes arbitrarily large, the current can arc across the capacitor, effectively ignoring its presence, and  $Z \cong \frac{R_1 R_2}{R_1 + R_2}$ .

➤  $V = I|Z|$

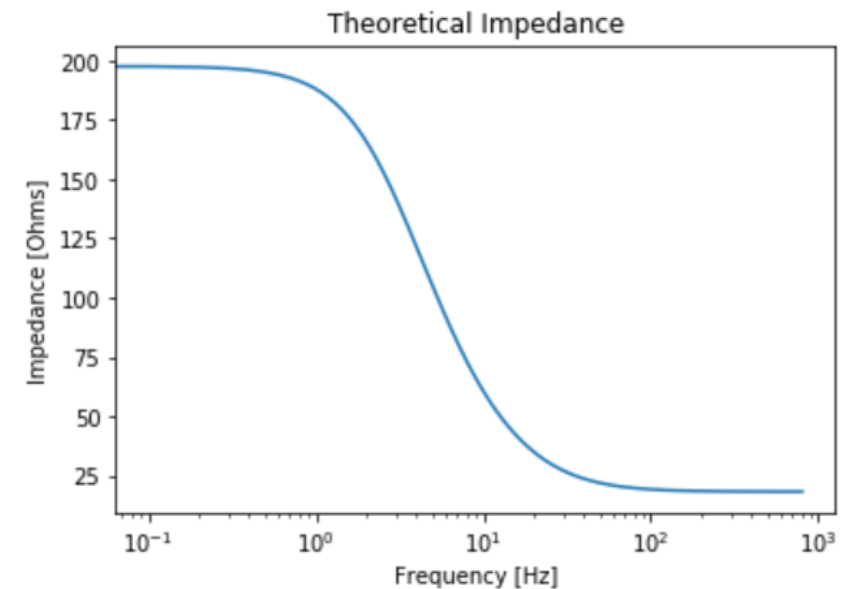

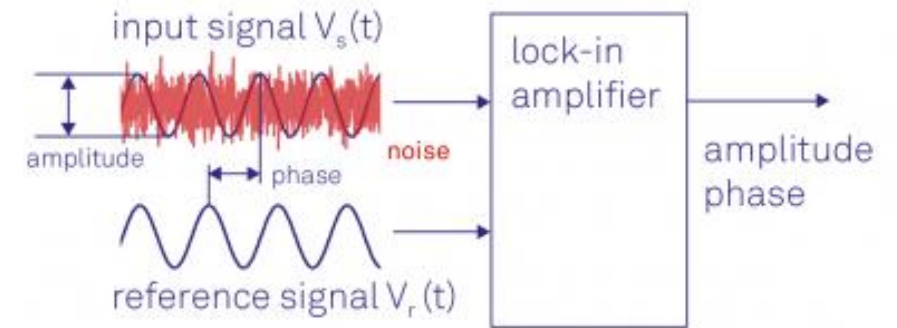
# Lock-In Amplifier



- Especially at low current, background noise conflicts with data
  - Need a way to remove unwanted signals
- One solution: Lock-in Amplifier
  - Phase sensitive detection / demodulation
  - Synchronizes internal oscillator to external reference signal
- Multiplies and integrates two signals (reference and input):
  - $A_{sig} \sin(\omega_{sig} + \phi_{sig}) \times A_{ref} \sin(\omega_{ref} + \phi_{ref})$
- Output becomes:
  - 0 for differing frequencies
  - $V_{out} = (1/2) V_{sig} V_{ref} \cos(\phi)$
- Result is isolation of signals with frequencies of interest, effectively reduces background noise


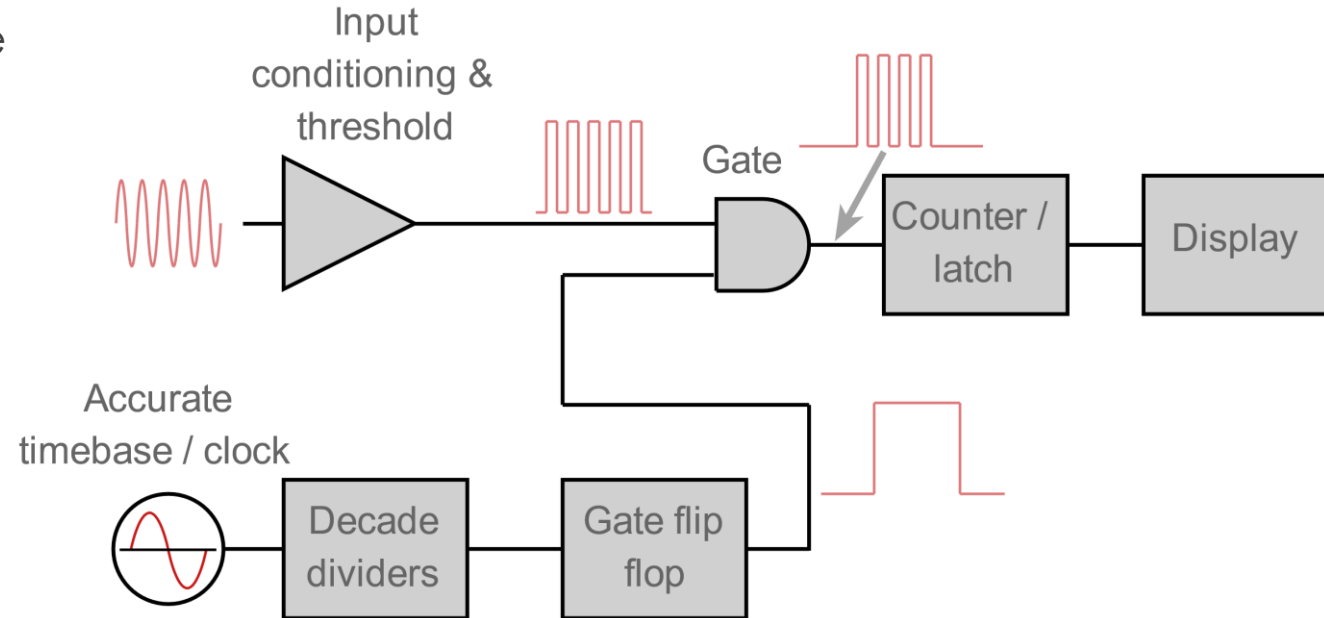
# Frequency Meter

- ▶ A digital frequency counter measures frequency by taking counts of a periodic function over a **gate time**.
- ▶ **Direct counting** methods measure how many times the voltage (or other property being measured) passes a given threshold.
- ▶ **Reciprocal** frequency counters measure the period of a cycle and take the inverse.
- ▶ A clock produces a signal which is divided by the **decade dividers** into the appropriate gate time.
- ▶ The “gate flip flop” receives this information and signals when the next set of counts should begin.
- ▶ The **latch** holds the last value so that it can continue to be displayed while the counter is updating based on a new set of data.



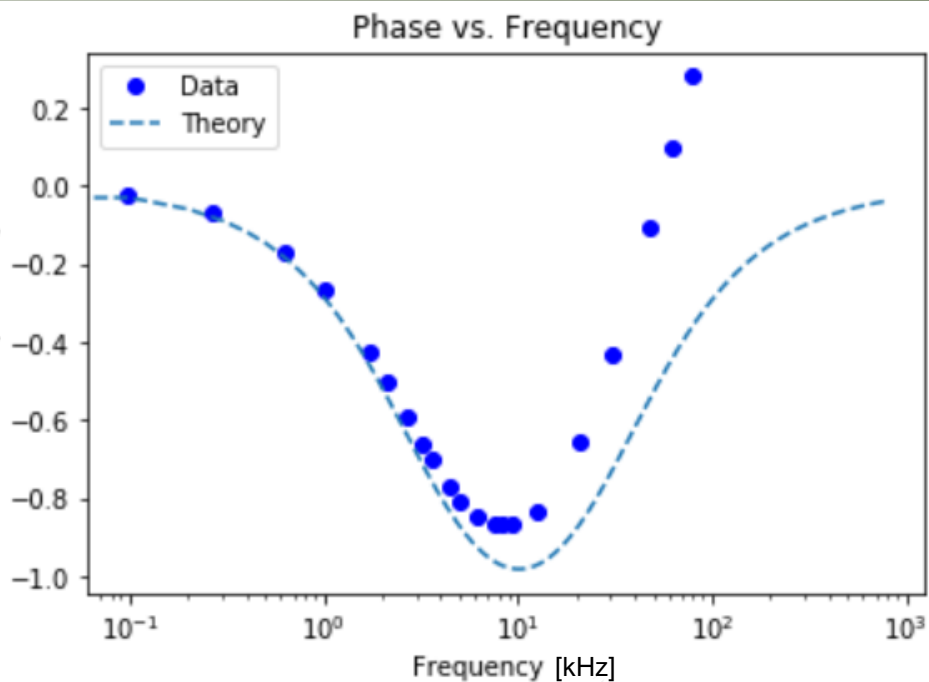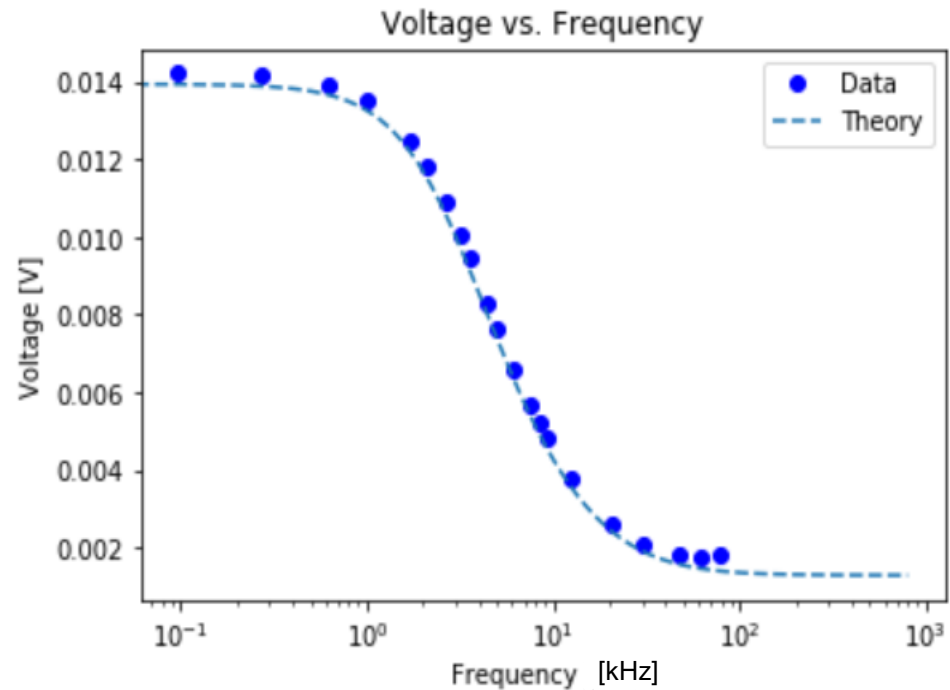

# Prediction vs. Data

## Voltage Data

- ▶ We see an almost perfect correlation here, especially in the center.
- ▶ Asymptotes match fairly well
- ▶ Standard deviation:  $8 \times 10^{-8} [\text{V}]$


## Phase Data

- ▶ The left half of the plot appears to be roughly correct.
- ▶ The dip occurs at the right point.
- ▶ We have positive phase; this should be impossible with an ideal circuit of our type
- ▶ Possible explanation: Something within the circuit is behaving as an inductor, producing a field opposing the current, causing the positive phase.
- ▶ Standard deviation: 0.05 [radians]

# Curve Fitting


- Assuming a circuit with the same arrangement but different component values, Python can be used to fit a curve and approximate unknown circuit values
- SciPy.curve\_fit() allows users to define a custom function with parameters to be optimized
- Values from curve\_fit
  - $R_0 = 6.82329841 \times 10^4$   
 $R_1 = 1.36179032 \times 10^3$   
 $R_2 = 1.00003488 \times 10^0$   
 $C = -2.20289657 \times 10^{-4}$
  - Covariance Matrix:
 

$7.29720286 \times 10^{21}$	$1.45637188 \times 10^{20}$	$2.08120685 \times 10^{14}$	$2.35187976 \times 10^{13}$
$1.45637188 \times 10^{20}$	$2.90661927 \times 10^{18}$	$4.15366154 \times 10^{12}$	$4.69386915 \times 10^{11}$
$2.07711078 \times 10^{14}$	$4.14548663 \times 10^{12}$	$2.78138962 \times 10^7$	$6.67042843 \times 10^5$
$2.35188426 \times 10^{13}$	$4.69387815 \times 10^{11}$	$6.68364286 \times 10^5$	$7.58012135 \times 10^4$
- Fit is close until higher frequency limit
  - Possible background inductance affecting derivation for  $V(f)$  due to affect on total system impedance

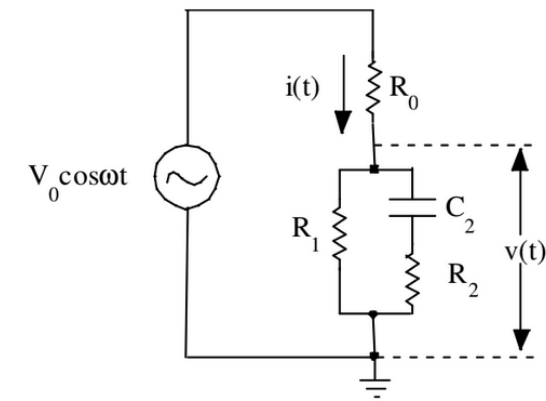

$$V = \frac{V_0}{R_0} R_1 \frac{\sqrt{(1 + (2\pi f)^2 C^2 R_2 (R_1 + R_2))^2 + (2\pi f C)^2}}{1 + (2\pi f)^2 C^2 (R_1 + R_2)^2}$$
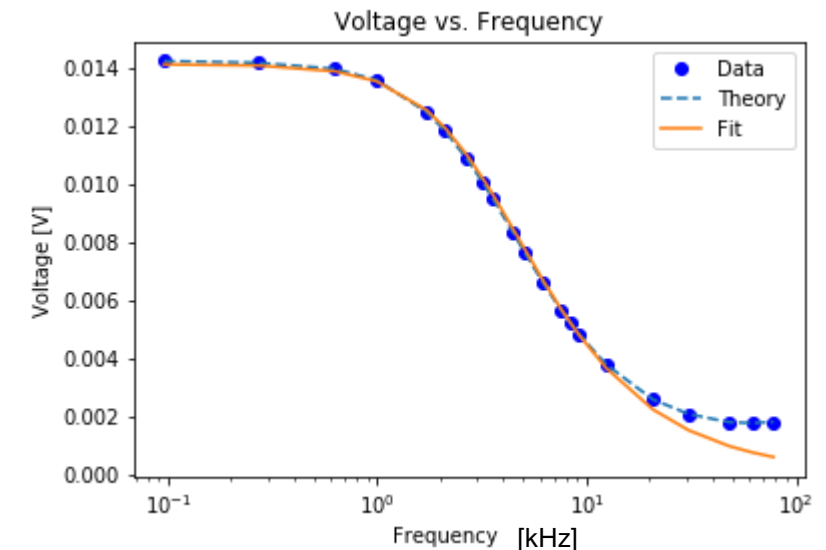
$$\phi = -\frac{2\pi f C}{1 + (2\pi f)^2 C^2 R_2 (R_1 + R_2)^2}$$





# References



- <https://www.instructables.com/id/Digital-Frequency-Counter/>
- <https://www.electronics-notes.com/articles/test-methods/frequency-counter-timer/how-does-a-frequency-counter-work-operation.php>