

Analysis - Impedance Spectroscopy

May 5, 2019

```
In [1]: #import stuff!
import numpy as np
from scipy.stats import chisquare
from scipy.optimize import curve_fit
import matplotlib.pyplot as plt
```

Theory

```
In [6]: #Setting up Constants
j = (-1)**(1/2)
R0 = 10020 #Voltage-Setting Resistor [Ohms]
R1 = 197.7 #Parallel Resistor [Ohms]
R2 = 20.0 #Series Resistor [Ohms]
C = 0.000238 #Capacitor [Farads]
V0_in = 0.707 #Voltage In [V]

#creating shorthands
R = R2/(R1+R2) #Based on equivalent resistance (unitless)
I0 = V0_in/R0 #I calculated from VAC [A]
wc = 1/((R1+R2)*C) #shorthand frequency constant [rad/s]

#Creating Arrays
f0 = [i/100 for i in range(80000)] #Creating a range of (linear) frequencies [Hz]

w0 = []
for i in f0:
    w0.append(2*np.pi*i)

In [7]: #Running Loops for Functions

#Impedance Function.
#Commented out because it is expressed always in terms of Real or Imaginary parts.

#Z = []
#for i in w:
#    Z.append(R1*(1+i**2*R2(R1+R2)-j*i*C*R1)/(1+i*2*C**2*(R1+R2)**2))
```

```

#Real(Z)
ReZ = []
for i in w0:
    ReZ.append(R1*(1+i**2*C**2*R2*(R1+R2))/(1+i**2*C**2*(R1+R2)**2))

#Imaginary(Z)
ImZ = []
for i in w0:
    ImZ.append(-R1*i*C*R1/(1+i**2*C**2*(R1+R2)**2))

#Phase
Ph = []
i = 0
while i < len(ImZ):
    Ph.append(np.arctan(ImZ[i]/ReZ[i]))
    i += 1

#|Z|
i = 0
MagZ = []
while i < len(ImZ):
    MagZ.append((ReZ[i]**2+ImZ[i]**2)**(1/2))
    i += 1

#Voltage
V0 = []
for i in MagZ:
    V0.append(I0*i)


```

In [8]: *#Impedance Theory*

```

plt.plot(f0,MagZ)
#plt.axis([0,100,0,200])
plt.xlabel('Frequency [Hz]')
plt.ylabel('Impedance [Ohms]')
plt.title('Theoretical Impedance')
plt.xscale('log')
plt.show()

```

 

Data

In [9]: *#Set up data. Keep data all in the same order! Also, make sure units are converted to .*

```
#frequency - kHz, must be converted
f_kHz = [96, 268, 630, 995, 1720, 2114, 2665, 3193, 3570, 4460, 5047, 6195, 7531, 8357]
#V_Orms - mV, must be converted
V_mV = [14.22, 14.16, 13.95, 13.56, 12.47, 11.81, 10.88, 10.05, 9.48, 8.32, 7.65, 6.60]
#phase - Degrees, must be converted
P_deg = [-1.3, -3.8, -9.9, -15.1, -24.3, -28.7, -33.8, -37.8, -40.2, -44.3, -46.3, -48.5, -49.8, -49.8]

P = [] #Phase in radians
for n in P_deg:
    P.append(2*np.pi*n/360)

V = [] #Voltage in Volts
for n in V_mV:
    V.append(n*10**-3)

P_inv = [] #negative of phase
for n in P:
    P_inv.append(-n)

f = []
```

```

for n in f_kHz:
    f.append(n/1000)

```

Curve Fitting

In [11]: *### Create Curve Fit*

```

def func(f,R0f,R1f,R2f,Cf):
    return (V0_in/R0f)*R1f*((1+(2*np.pi*f)**2*Cf**2*R2f*(R1f+R2f))**2+(2*np.pi*f*Cf)**2)

popt, pcov = curve_fit(func,f,V)
print(popt)

### Plotting - Voltage vs Frequency

#x = freq
#y = [func(i,popt[0],popt[1],popt[2],popt[3]) for i in freq]


fig, sp = plt.subplots()

plt.title('Voltage vs. Frequency')
sp.plot(f,V,'bo',label='Data')
#sp.plot(f0,V0,'--',label='Theory') #uncomment to view theory
#sp.plot(w0,V0,'r--',label='Theory (Angular)') #uncomment to check angular vs linear
#sp.plot(f,func(f,*parameter),'-',label='Fit') #uncomment when curve fit is fixed.
legend = sp.legend(loc='upper right')
plt.xlabel('Frequency [Hz]')
plt.ylabel('Voltage [V]')
plt.xscale('log')

plt.show()

```
 
```
[-139.64558599 -1.74744466 -12.29023508 -180.88587252]
```



In [12]: *#Create Curve Fit*

```
def func(f,R0f,R1f,R2f,Cf):
    return np.arctan(-2*np.pi*f*Cf/(1+(2*np.pi*f)**2*Cf**2*(R1f+R2f)**2))
popt, pcov = curve_fit(func,f,P)
parameter, covariance_matrix = curve_fit(func,f,P)

#Plotting - Phase vs Frequency


fig, sp = plt.subplots()

plt.title('Phase vs. Frequency')
sp.plot(f,P,'bo',label='Data')
#sp.plot(f0,Ph,'--',label='Theory') #uncomment to view theory
#sp.plot(w0,Ph,'r--',label='Theory (Angular)') #uncomment to check for angular vs lin
#sp.plot(f,func(f,*parameter),'-',label='Fit') #uncomment when curve fit is working
legend = sp.legend(loc='upper left')
plt.xlabel('Frequency [Hz]')
plt.ylabel('Phase (Radians)')
plt.xscale('log')

plt.show()
```

K:\Anaconda\lib\site-packages\scipy\optimize\minpack.py:794: OptimizeWarning: Covariance of the

```
category=OptimizeWarning)
```

 

Theory vs. Data

```
In [13]: #Running Loops for Expected values - we will need these for chi squared.  
         #These are based on theory, not on curve fitting.
```

```
         #Real(Z)
```

```
         ReZ_exp = []
```

```
         for n in f:
```

```
             ReZ_exp.append(R1*(1+(2*np.pi*n)**2*C**2*R2*(R1+R2))/(1+(2*np.pi*n)**2*C**2*(R1+R2)))
```

```
         #Imaginary(Z)
```

```
         ImZ_exp = []
```

```
         for n in f:
```

```
             ImZ_exp.append(-R1*(2*np.pi*n)*C*R1/(1+(2*np.pi*n)**2*C**2*(R1+R2)**2))
```

```
         #Phase
```

```
         P_exp = []
```

```
         i = 0
```

```
         while i < len(ImZ_exp):
```

```
             P_exp.append(np.arctan(ImZ_exp[i]/ReZ_exp[i]))
```

```
             i += 1
```

```

#|Z|
i = 0
MagZ_exp = []
while i < len(ImZ_exp):
    MagZ_exp.append((ReZ_exp[i]**2+ImZ_exp[i]**2)**(1/2))
    i += 1

#Voltage
V_exp = []
for n in MagZ_exp:
    V_exp.append(I0*n)

```

In [14]: *#Plotting - Phase vs Frequency*

```


fig, sp = plt.subplots()

plt.title('Phase vs. Frequency')
sp.plot(f,P,'bo',label='Data')
sp.plot(f0,Ph,'--',label='Theory')
#sp.plot(f,P_exp) #checking that expected value calculations are correct.
legend = sp.legend(loc='upper left')
plt.xlabel('Frequency [Hz]')
plt.ylabel('Phase (Radians)')
plt.xscale('log')

plt.show()

chisquare(P,P_exp)

```

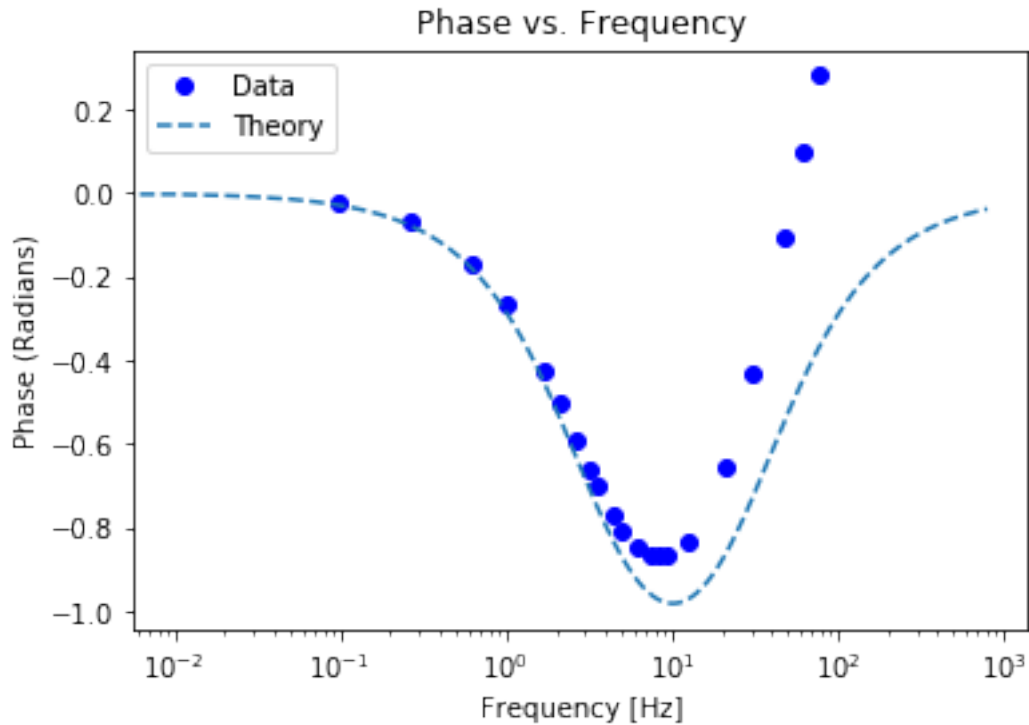

Out[14]: Power_divergenceResult(statistic=-2.419738578497731, pvalue=1.0)


In [15]: *#plotting - Voltage vs Frequency*

```
fig, sp = plt.subplots()

plt.title('Voltage vs. Frequency')
sp.plot(f,V,'bo',label='Data')
sp.plot(f0,V0,'--',label='Theory')
#sp.plot(f,V_exp) #checking that expected value calculations are correct
legend = sp.legend(loc='upper right')
plt.xlabel('Frequency [Hz]')
plt.ylabel('Voltage [V]')
plt.xscale('log')

plt.show()

chisquare(V,V_exp)
```
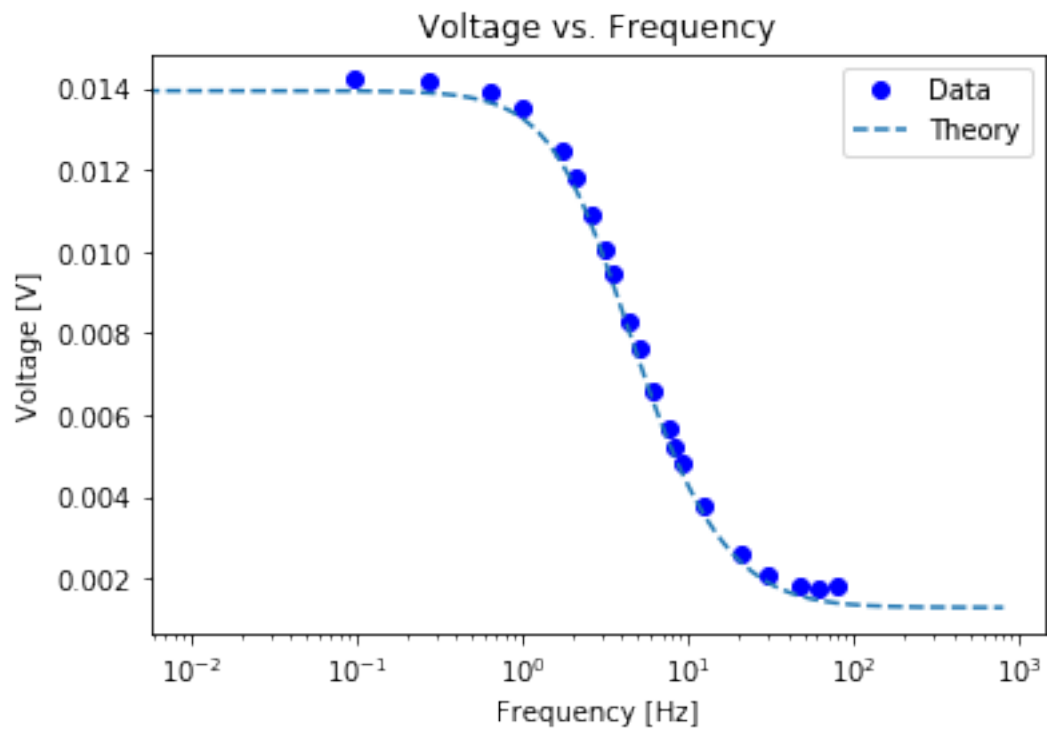
```
Out[15]: Power_divergenceResult(statistic=0.00042573181659759905, pvalue=1.0)
```

```
In [ ]:
```